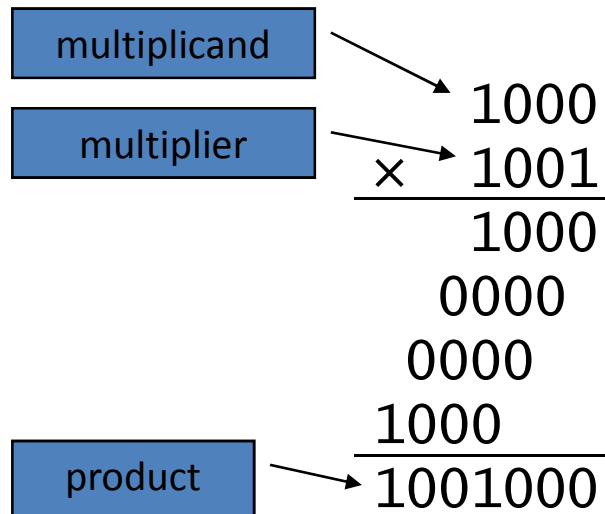



# Multiplication
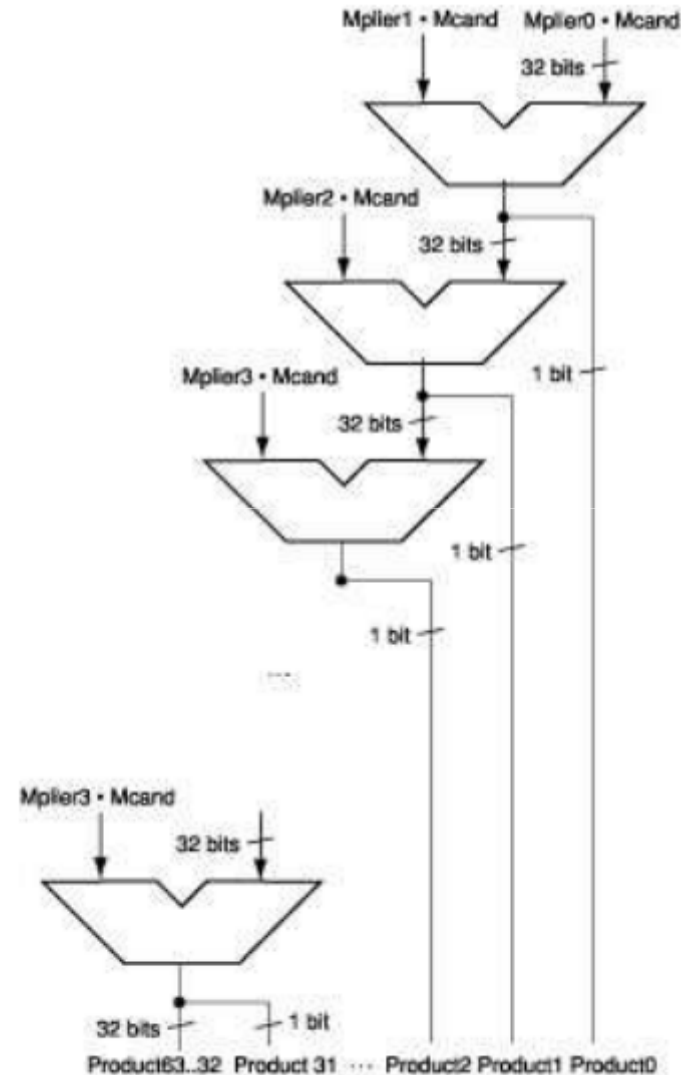
# Multiplication



- Start with long-multiplication approach



Length of product is the sum of operand lengths




# Multiplication of positive numbers

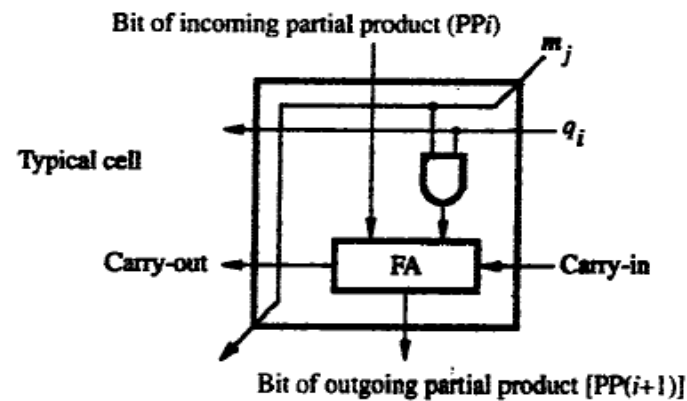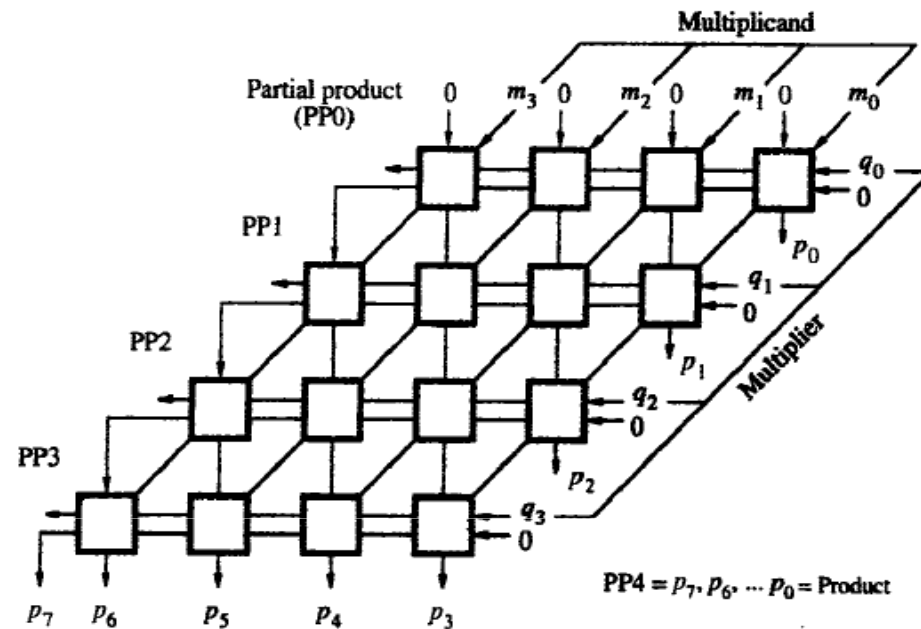


Combinational logic & Array Implementation

# Multiplication of positive numbers

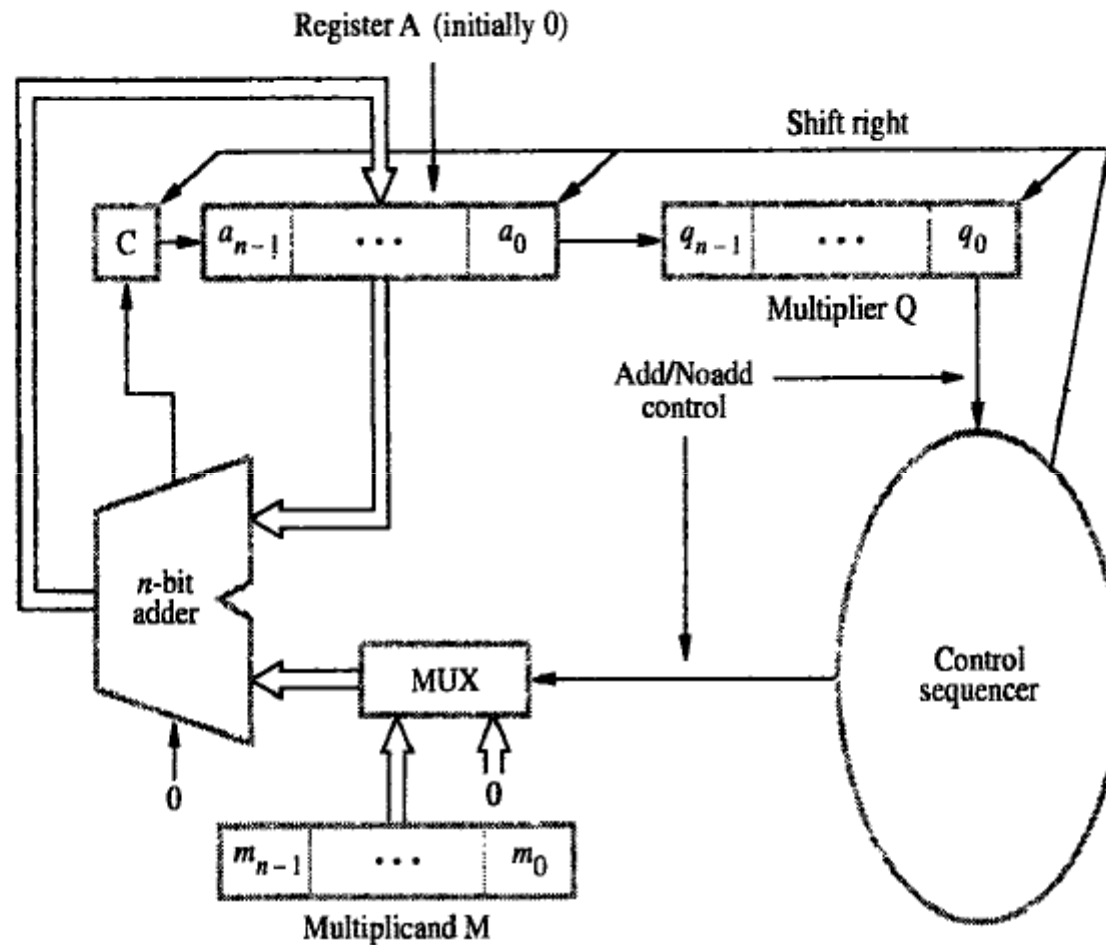


Sequential circuit binary multiplier-Register Configuration

# Multiplication of positive numbers

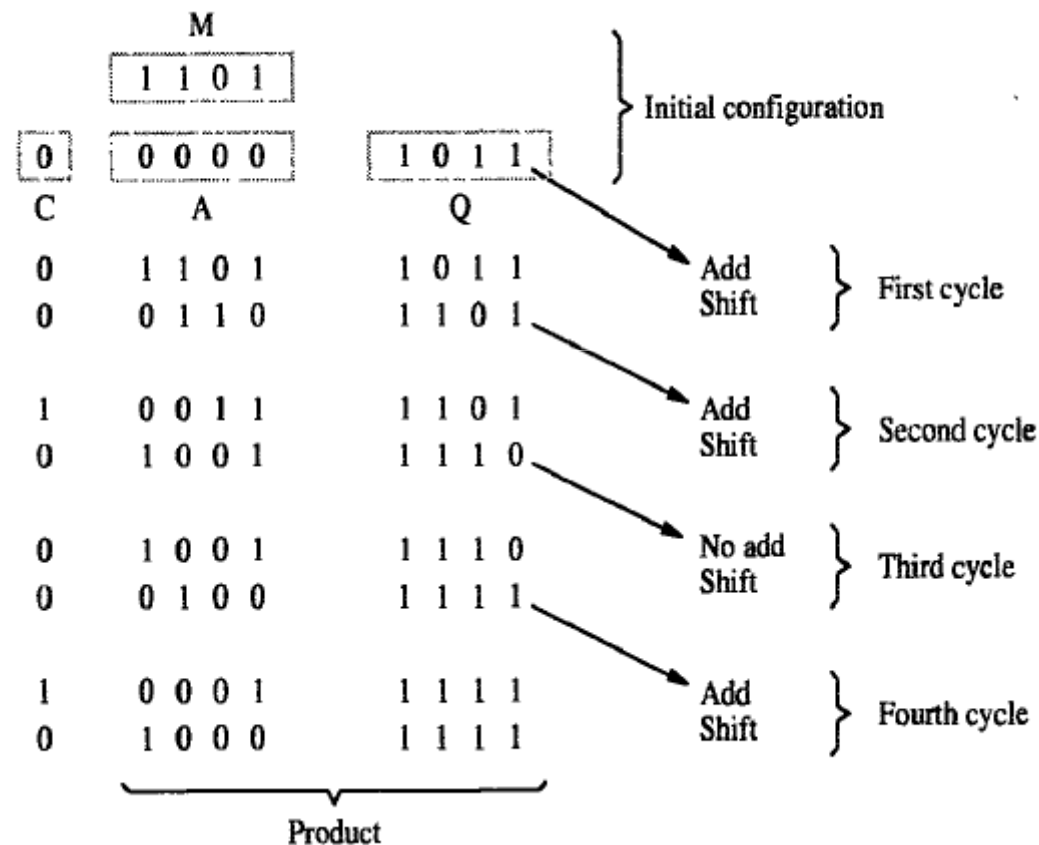

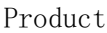Sequential circuit binary multiplier- Multiplication Example



6

# Carry-Save Addition of Summands


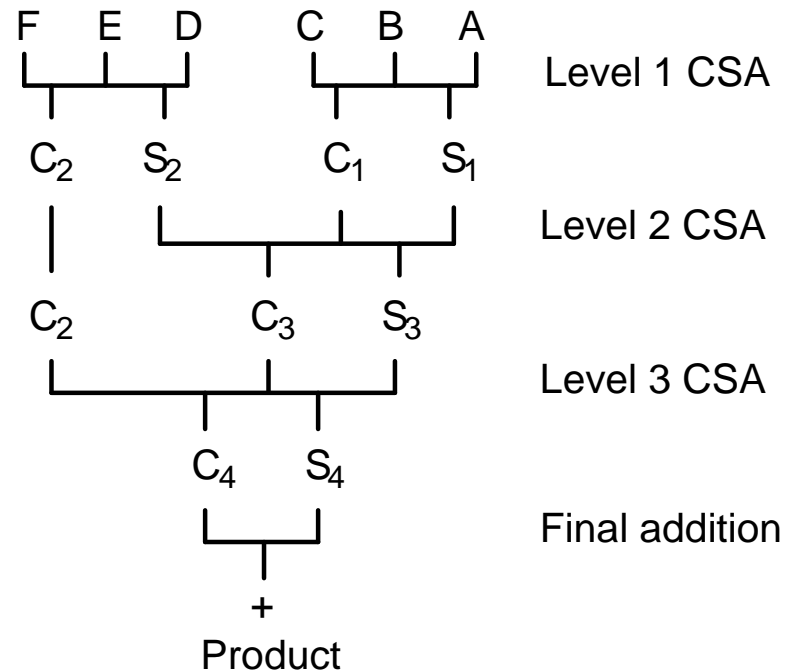



Figure 6.19. Schematic representation of the carry-save addition operations in Figure 6.18.
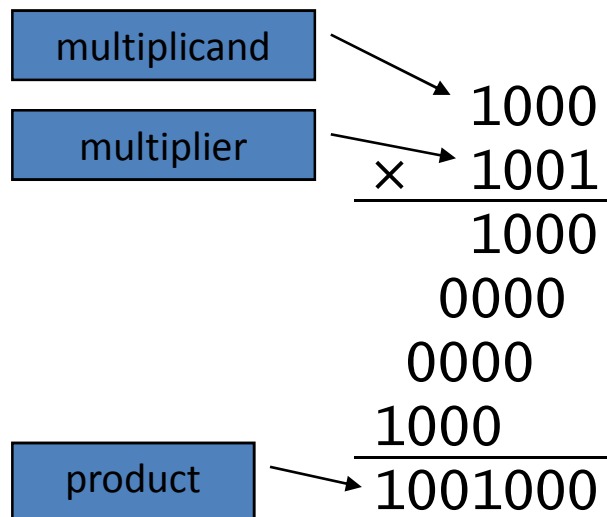
# Multiplication

- Start with long-multiplication approach




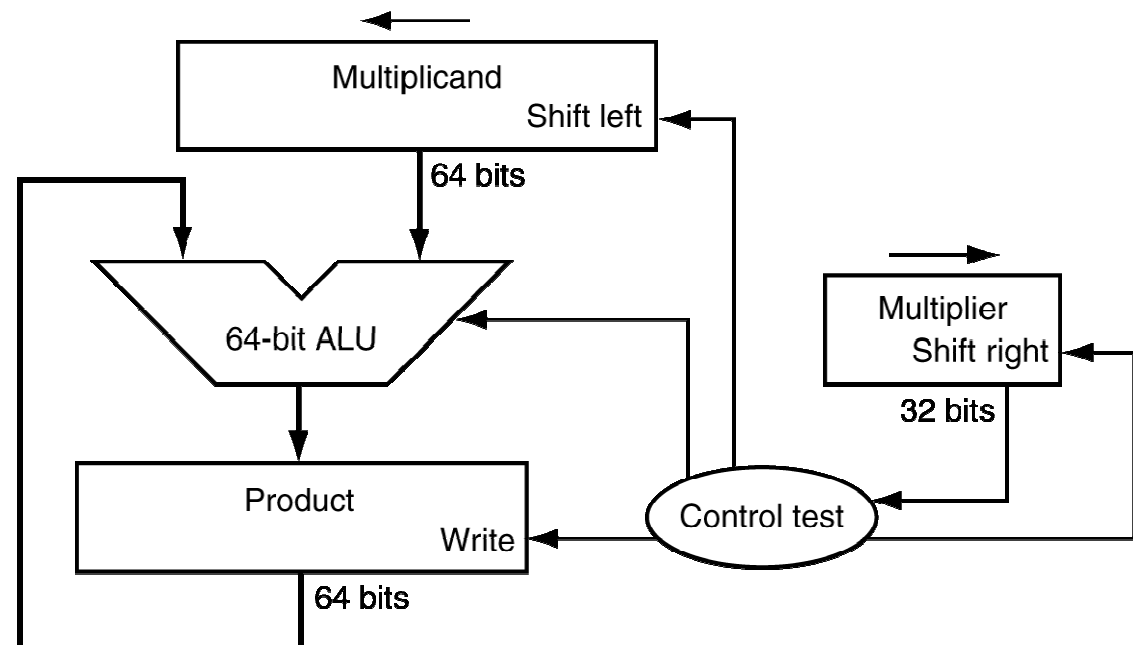Length of product is the sum of operand lengths







# Multiplication Hardware

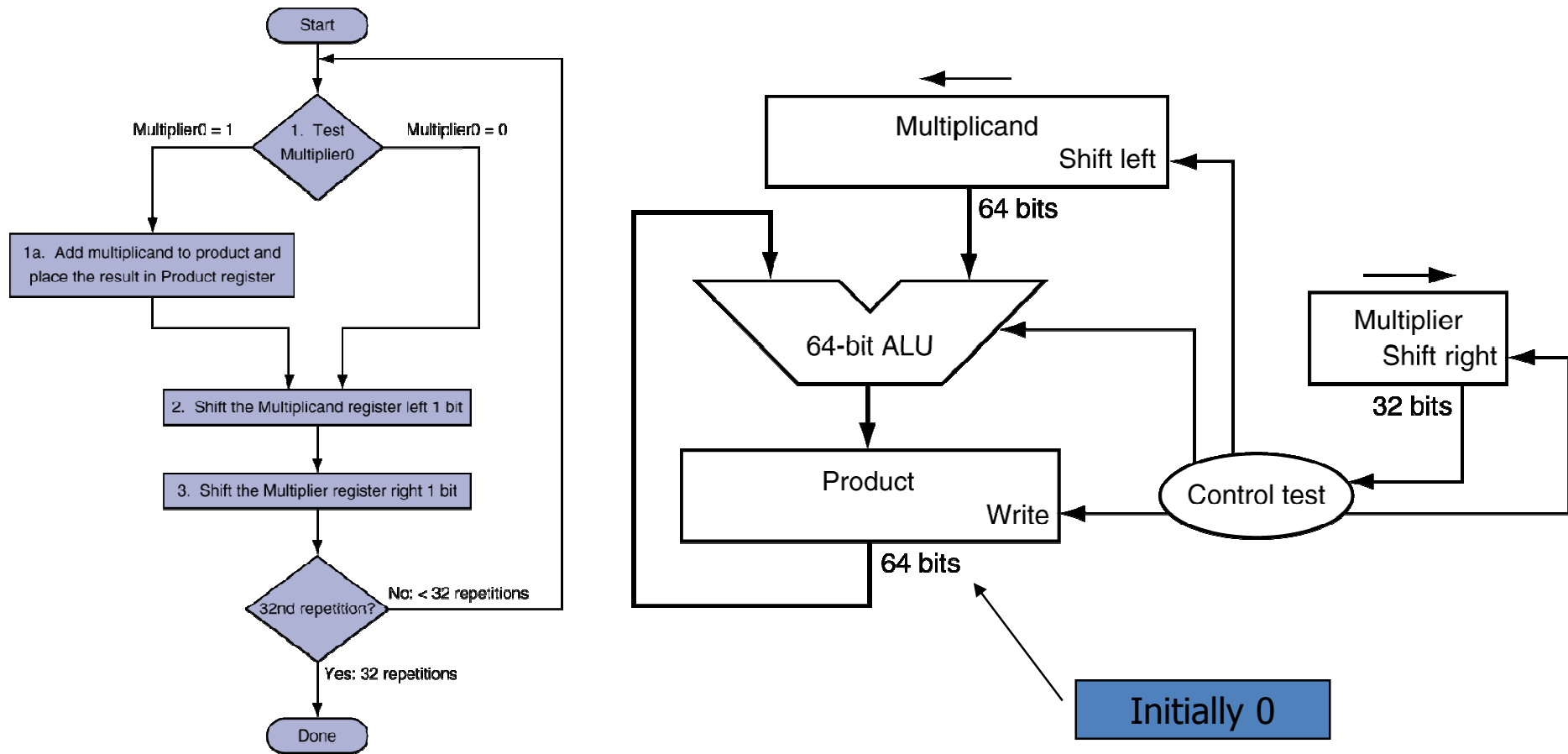

# Second Version

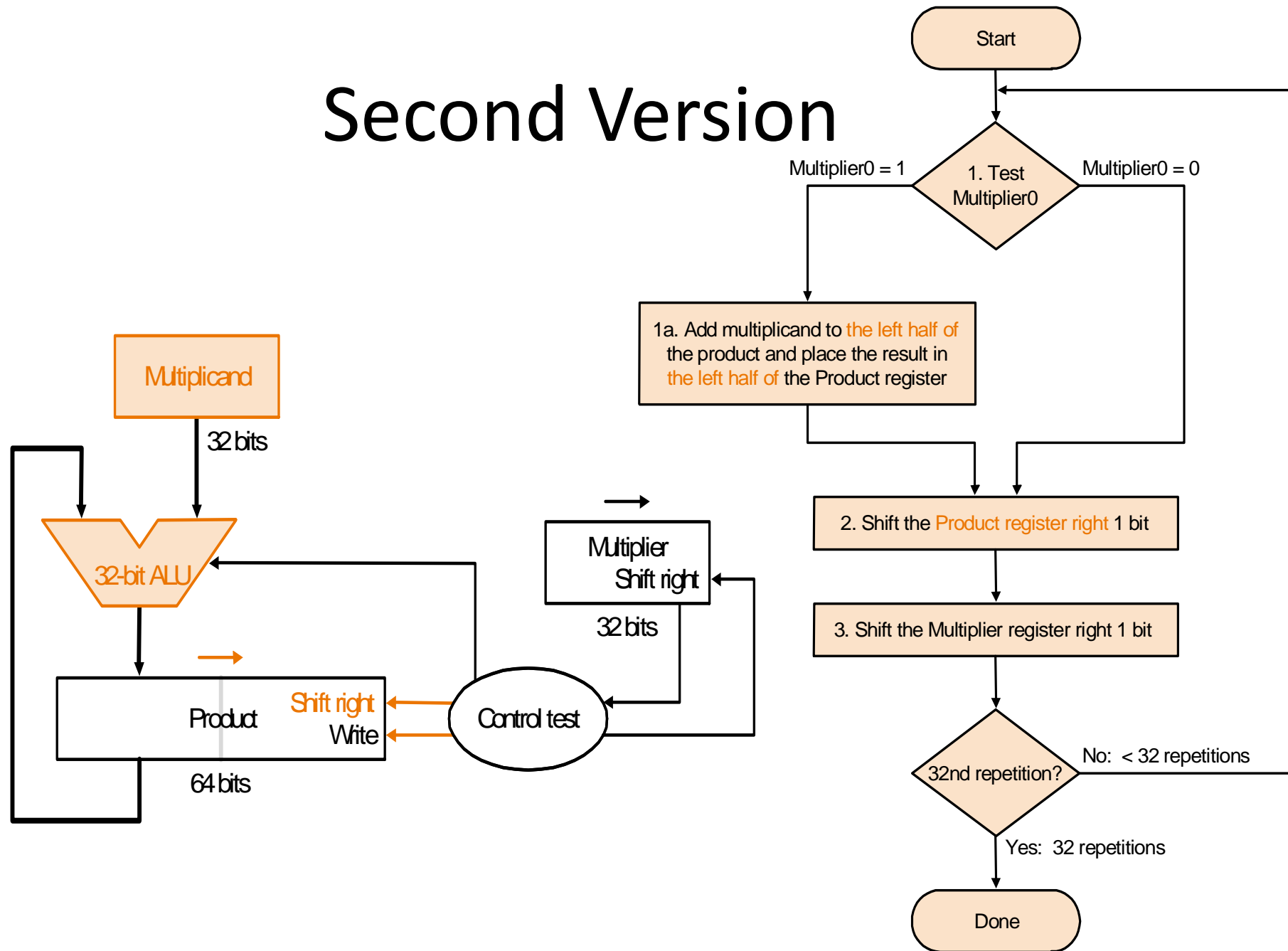

# Final Version

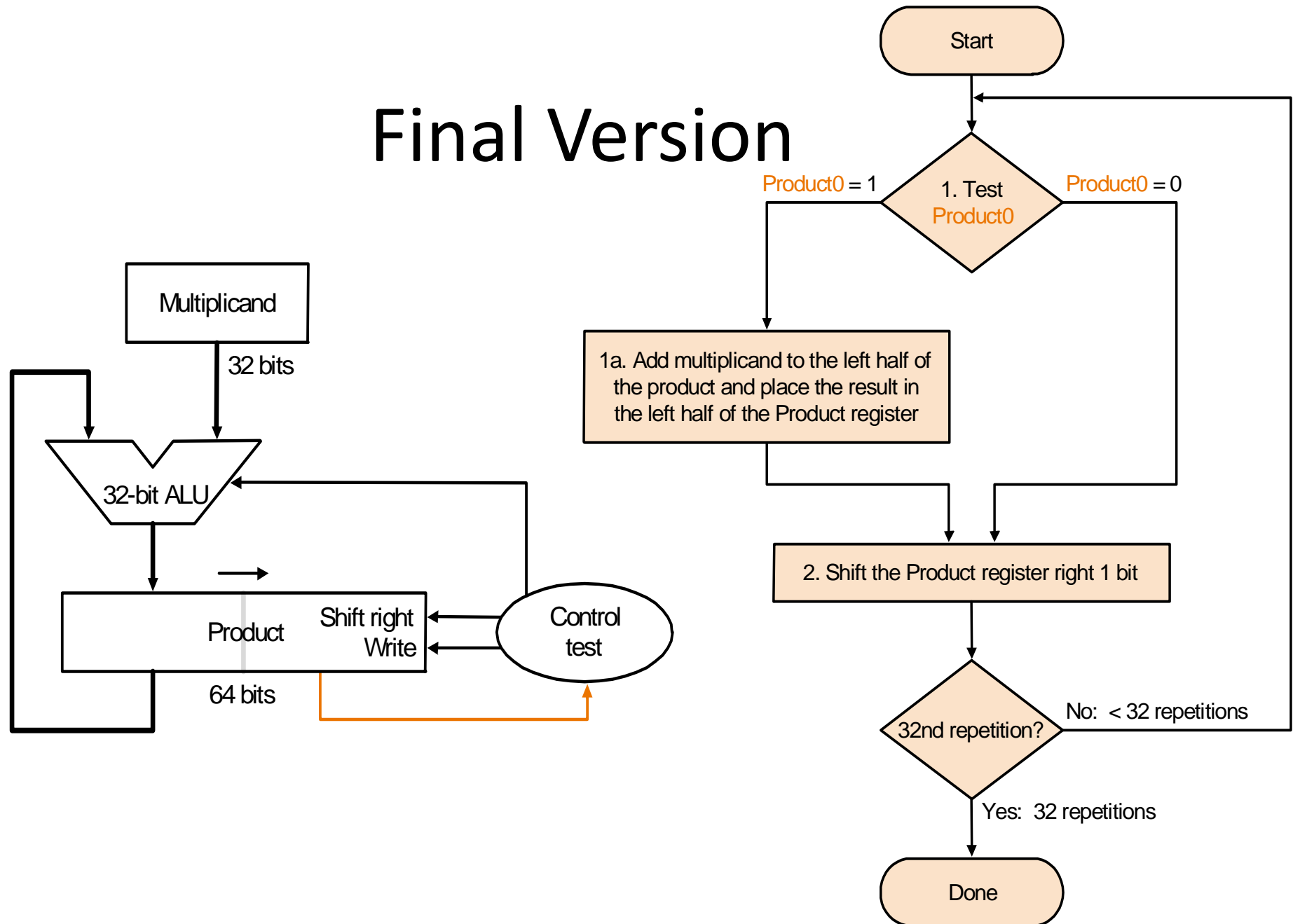

# Signed Multiplication

# Signed Multiplication

- Considering 2's-complement signed operands, what will happen to  $(-13) \times (+11)$  if following the same method of unsigned multiplication?

						1	0	0	1	1	<b>(- 13)</b>
						0	1	0	1	1	<b>(+ 11)</b>
						<hr/>					
					1	1	0	0	1	1	
				1	1	0	0	1	1		
			1	1	0	0	0	0			
		1	1	0	0	1	1				
	1	1	0	0	0	0					
	1	1	0	1	1	1	0	0	0	1	<b>(- 143)</b>

**SIGN EXTENSION IS SHOWN IN BLUE**

Figure 6.8. Sign extension of negative multiplicand.

# Signed Multiplication

- For a negative multiplier, a straightforward solution is to form the 2's-complement of both the multiplier and the multiplicand and proceed as in the case of a positive multiplier.
- This is possible because complementation of both operands does not change the value or the sign of the product.
- A technique that works equally well for both negative and positive multipliers – Booth algorithm.

# Booth Algorithm

- Consider in a multiplication, the multiplier is positive 0011110, how many appropriately shifted versions of the multiplicand are added in a standard procedure?

$$\begin{array}{r}
 \begin{array}{cccccccc}
 & & & & 0 & 1 & 0 & 1 & 1 & 0 & 1 \\
 & & & & 0 & 0 & +1 & +1 & +1 & +1 & 0 \\
 \hline
 & & & & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 & & & 0 & 1 & 0 & 1 & 1 & 0 & 1 & \\
 & & 0 & 1 & 0 & 1 & 1 & 0 & 1 & & \\
 & 0 & 1 & 0 & 1 & 1 & 0 & 1 & & & \\
 & & 0 & 1 & 0 & 1 & 1 & 0 & 1 & & \\
 & & & 0 & 0 & 0 & 0 & 0 & 0 & 0 & \\
 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & & & \\
 \hline
 0 & 0 & 0 & 1 & 0 & 1 & 0 & 1 & 0 & 0 & 0 & 1 & 1 & 0
 \end{array}
 \end{array}$$

# Booth Algorithm

- Since  $0011110 = 0100000 - 0000010$ , if we use the expression to the right, what will happen?

								0	1	0	1	1	0	1
								0	+1	0	0	0	-1	0
								<hr/>						
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	1	1	1	1	0	1	0	0	1	1	← 2's complement of the multiplicand
0	0	0	0	0	0	0	0	0	0	0	0	0	0	
0	0	0	0	0	0	0	0	0	0	0	0	0	0	
0	0	0	0	0	0	0	0	0	0	0	0	0	0	
0	0	0	1	0	1	1	0	1						
0	0	0	0	0	0	0	0	0						
<hr/>								0	0	0	1	0	1	0



# Booth Algorithm

- In general, in the Booth scheme, -1 times the shifted multiplicand is selected when moving from 0 to 1, and +1 times the shifted multiplicand is selected when moving from 1 to 0, as the multiplier is scanned from right to left.

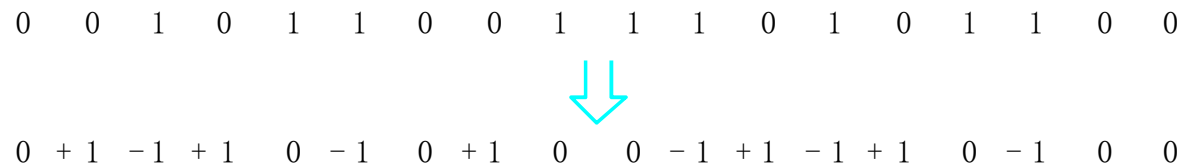


Figure 6.10. Booth recoding of a multiplier.

# Booth Algorithm

$\begin{array}{r} 01101 \quad (+13) \\ 11010 \quad (-6) \\ \hline \end{array}$	$\Rightarrow$	<table style="border-collapse: collapse;"> <tr> <td style="text-align: right; padding-right: 10px;"> <math display="block">\begin{array}{r} 01101 \\ 0-1+1-10 \\ \hline \end{array}</math> </td> <td style="text-align: left;"> <math display="block">\begin{array}{r} 00000 \\ 11111 \\ 00001 \\ 11100 \\ 00000 \\ \hline 1110110010 \quad (-78) \end{array}</math> </td> </tr> </table>	$\begin{array}{r} 01101 \\ 0-1+1-10 \\ \hline \end{array}$	$\begin{array}{r} 00000 \\ 11111 \\ 00001 \\ 11100 \\ 00000 \\ \hline 1110110010 \quad (-78) \end{array}$
$\begin{array}{r} 01101 \\ 0-1+1-10 \\ \hline \end{array}$	$\begin{array}{r} 00000 \\ 11111 \\ 00001 \\ 11100 \\ 00000 \\ \hline 1110110010 \quad (-78) \end{array}$			

Figure 6.11. Booth multiplication with a negative multiplier.

# Booth Algorithm

Multiplier		Version of multiplicand selected by bit
Bit $i$	Bit $i-1$	
0	0	0 $\times M$
0	1	+1 $\times M$
1	0	-1 $\times M$
1	1	0 $\times M$


Figure 6.12. Booth multiplier recoding table.

# Booth Algorithm

- Best case – a long string of 1's (skipping over 1s)
- Worst case – 0's and 1's are alternating


Worst-case multiplier

0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1



Ordinary multiplier

1	1	0	0	0	1	0	1	1	0	1	1	1	1	0	0
0	-1	0	0	+1	-1	+1	0	-1	+1	0	0	0	-1	0	0




Good multiplier

0	0	0	0	1	1	1	1	1	0	0	0	0	1	1	1
0	0	0	+1	0	0	0	0	-1	0	0	0	+1	0	0	-1

# Fast Multiplication
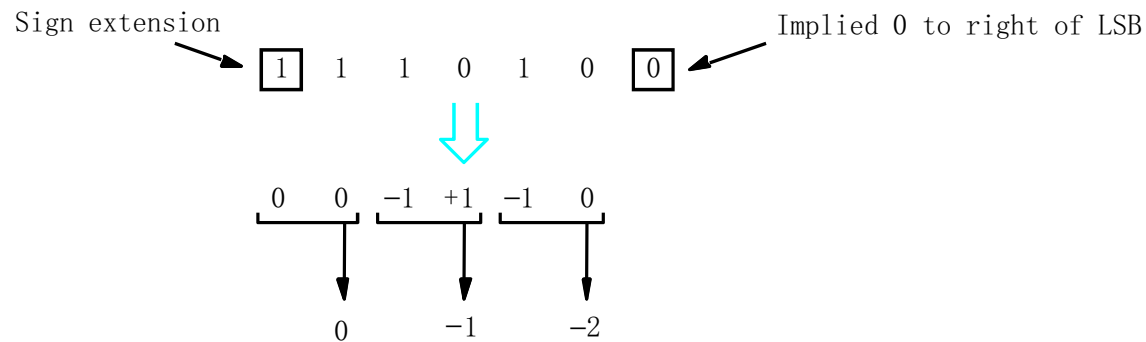
# Bit-Pair Recoding of Multipliers

- Bit-pair recoding halves the maximum number of summands (versions of the multiplicand).



(a) Example of bit-pair recoding derived from Booth recoding

# Bit-Pair Recoding of Multipliers

Multiplier bit-pair		Multiplier bit on the right	Multiplicand selected at position $i$
$i+1$	$i$	$i-1$	
0	0	0	0 $\times M$
0	0	1	+ 1 $\times M$
0	1	0	+ 1 $\times M$
0	1	1	+ 2 $\times M$
1	0	0	- 2 $\times M$
1	0	1	- 1 $\times M$
1	1	0	- 1 $\times M$
1	1	1	0 $\times M$

(b) Table of multiplicand selection decisions

# Bit-Pair Recoding of Multipliers

0 1 1 0 1 (+13)	0 1 1 0 1
' 1 1 0 1 0 (-6)	0 -1 +1 -1 0
	0 0 0 0 0
	1 1 1 1 1 0 0 1 1
	0 0 0 0 1 1 0 1
	1 1 1 0 0 1 1
	0 0 0 0 0 0
	1 1 1 0 1 1 0 0 1 0 (-78)

0 1 1 0 1	0 1 1 0 1
0 -1 -2	0 -1 -2
1 1 1 1 1 0 0 1 1 0	0 0 1 1 0
1 1 1 1 0 0 1 1	0 0 1 1
0 0 0 0 0 0	0 0 0 0
1 1 1 0 1 1 0 0 1 0	

Figure 6.15. Multiplication requiring only  $n/2$  summands.





# Carry-Save Addition of Summands

$$\begin{array}{rcccc}
 & & 1 & 1 & 0 & 1 & & (13) \text{ Multiplicand M} \\
 & & & & & & & \\
 & & 1 & 0 & 1 & 1 & & (11) \text{ Multiplier Q} \\
 & & & & & & & \\
 \hline
 & & 1 & 1 & 0 & 1 & & \\
 & & & & & & & \\
 & & 1 & 1 & 0 & 1 & & \\
 & & & & & & & \\
 & 0 & 0 & 0 & 0 & & & \\
 & & & & & & & \\
 & 1 & 1 & 0 & 1 & & & \\
 & & & & & & & \\
 \hline
 1 & 0 & 0 & 0 & 1 & 1 & 1 & 1 & (143) \text{ Product P}
 \end{array}$$

(a) Manual multiplication algorithm


# Carry-Save Addition of Summands

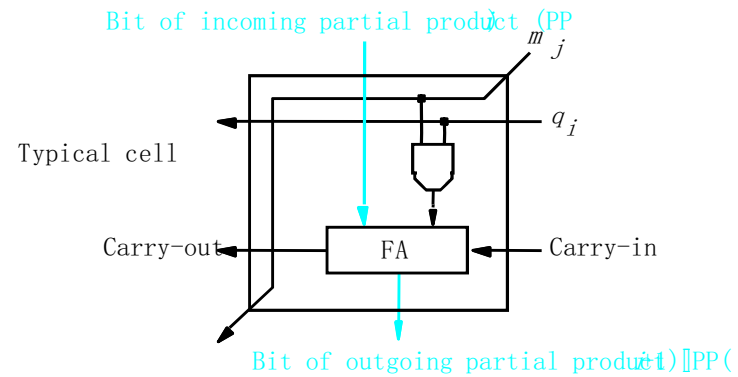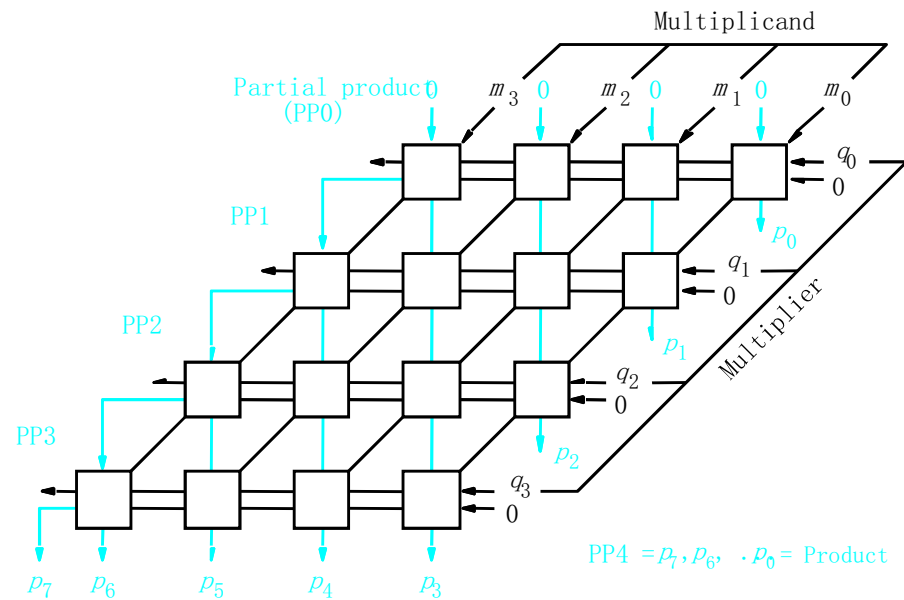

(b) Array implementation


# Carry-Save Addition of Summands

- CSA speeds up the addition process.

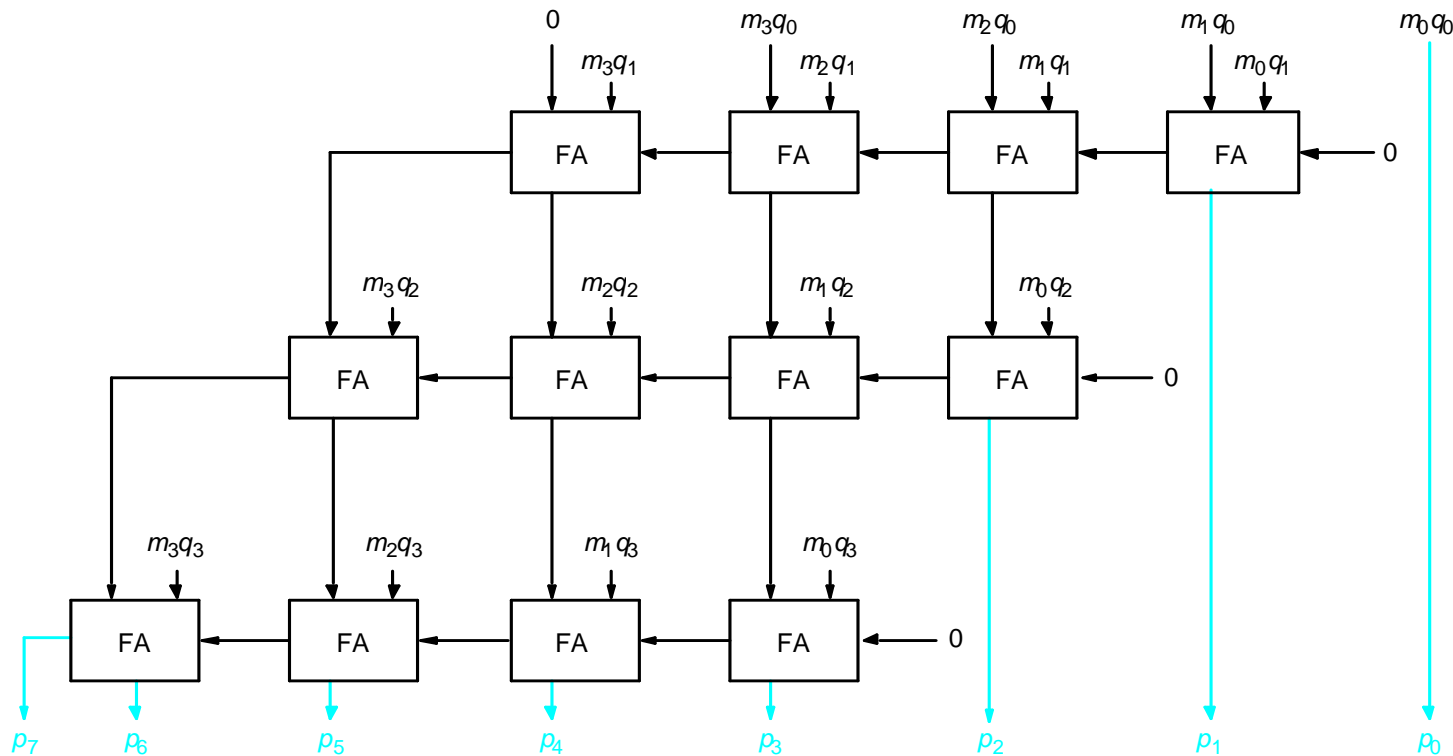

(a) Ripple-carry array (Figure 6.6 structure)

# Carry-Save Addition of Summands

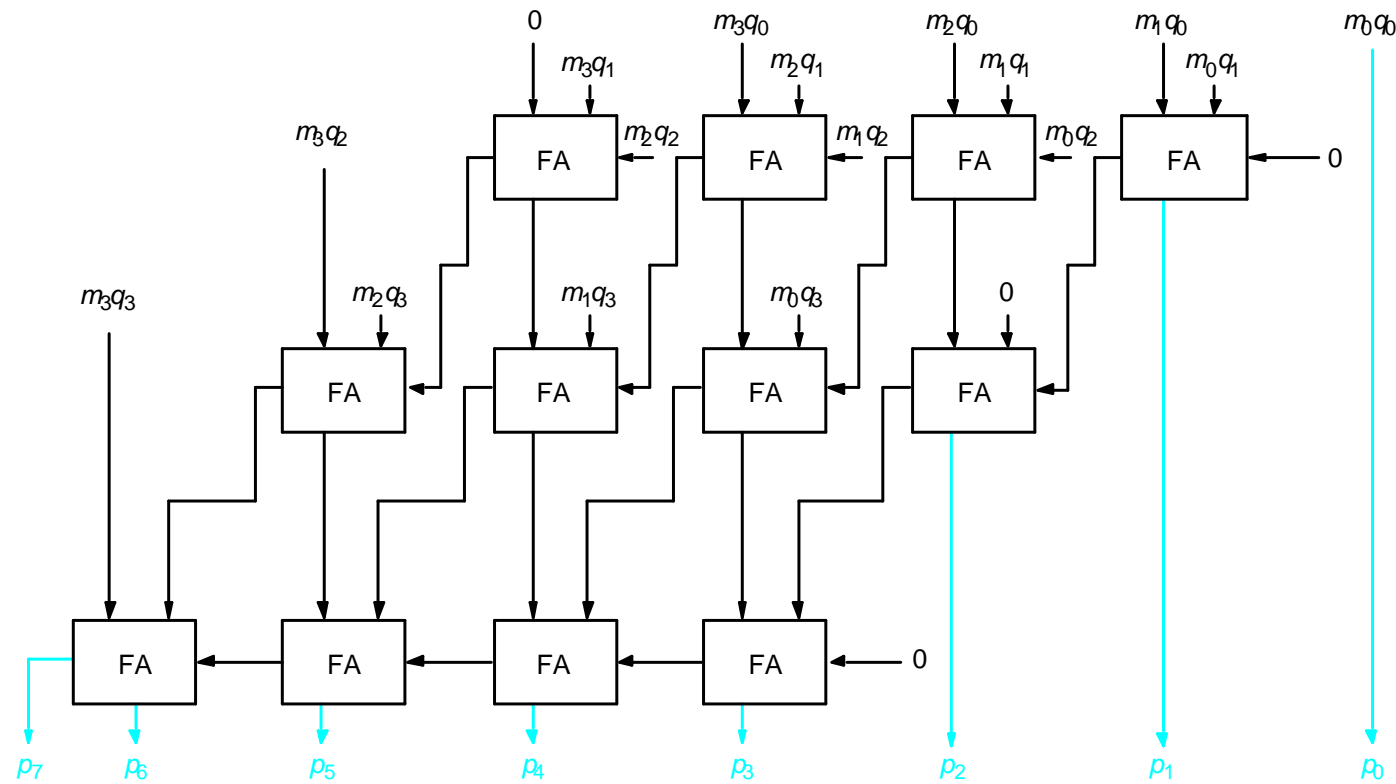

(b) Carry-save array

Figure 6.16. Ripple-carry and carry-save arrays for the multiplication operation  $M \times Q = P$  for 4-bit operands.

# Carry-Save Addition of Summands

- The delay through the carry-save array is somewhat less than delay through the ripple-carry array. This is because the S and C vector outputs from each row are produced in parallel in one full-adder delay.
- Consider the addition of many summands, we can:
  - Group the summands in threes and perform carry-save addition on each of these groups in parallel to generate a set of S and C vectors in one full-adder delay
  - Group all of the S and C vectors into threes, and perform carry-save addition on them, generating a further set of S and C vectors in one more full-adder delay
  - Continue with this process until there are only two vectors remaining
  - They can be added in a RCA or CLA to produce the desired product

# Carry-Save Addition of Summands

						1	0	1	1	0	1	(45)	M
					x	1	1	1	1	1	1	(63)	Q
						1	0	1	1	0	1	A	
				1		0	1	1	0	1		B	
			1	0		1	1	0	1			C	
		1	0	1		1	0	1				D	
	1	0	1	1		0	1					E	
1	0	1	1	0		1						F	
1	0	1	1	0	0	0	1	0	0	1	1	(2,835)	Product

Figure 6.17. A multiplication example used to illustrate carry-save addition as shown in Figure 6.18.